

Technische Informatik: Abgabe 8


Michael Mardaus

Andrey Tyukin

19. Dezember 2013


Exercise 8.1 (JK Flipflop Ringcounter)

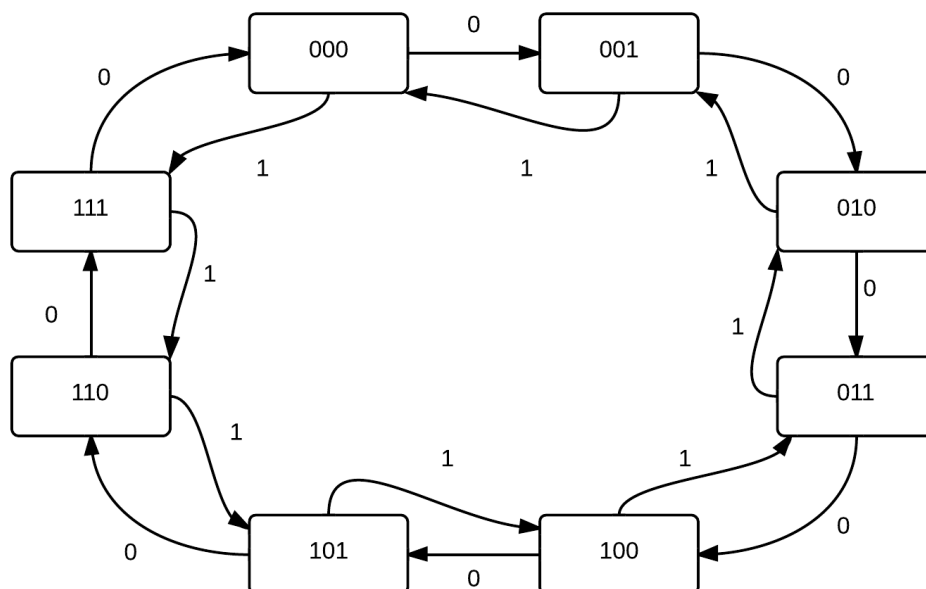a) We want to model a ring-counter that counts forwards if the input w is 0, and backwards if w is 1. It can be modeled by a Moore-automaton (the output depends only on the state). The state diagram looks as follows:



State diagram for the ring-counter. Output is omitted, it's just equal to the node index.

Same in table-form:

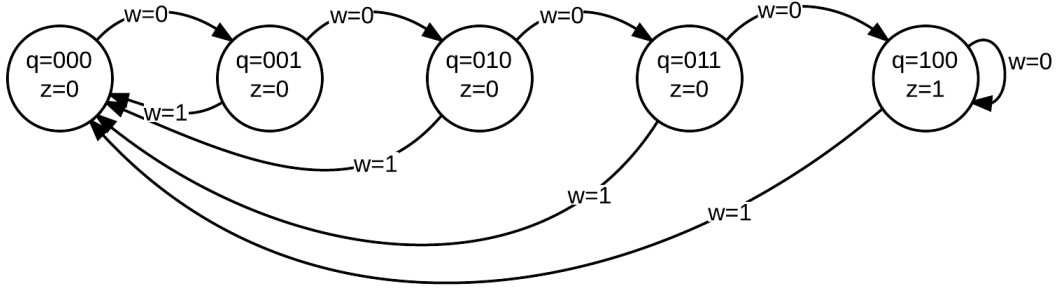

This leads to these K-maps:

J_0 wy_2	y_1y_0			
	00	01	11	01
00	1	d	d	1
01		d	d	d
11		d	d	d
10		d	d	

J_1 wy_2	y_1y_0			
	00	01	11	01
00		1	d	d
01		d	d	d
11		d	d	d
10			d	d

J_2 wy_2	y_1y_0			
	00	01	11	01
00			1	
01	d	d	d	d
11	d	d	d	d
10				

K_0 wy_2	y_1y_0			
	00	01	11	01
00	d	1	1	d
01	d	d	d	d
11	d	d	d	d
10	d	1	1	d


K_1 wy_2	y_1y_0			
	00	01	11	01
00	d	d	1	
01	d	d	d	d
11	d	d	d	d
10	d	d	d	1

K_2 wy_2	y_1y_0			
	00	01	11	01
00	d	d	d	d
01		d	d	d
11	1	d	d	d
10	d	d	d	d

These K-maps lead us to:

$$\begin{aligned}
 J_0 &= \bar{w}\bar{y}_2 \\
 J_1 &= \bar{w}y_0 \\
 J_2 &= \bar{w}y_1y_0 \\
 K_0 &= 1 \\
 K_1 &= w + y_0 \\
 K_2 &= w
 \end{aligned}$$

Which brings us to this circuit:

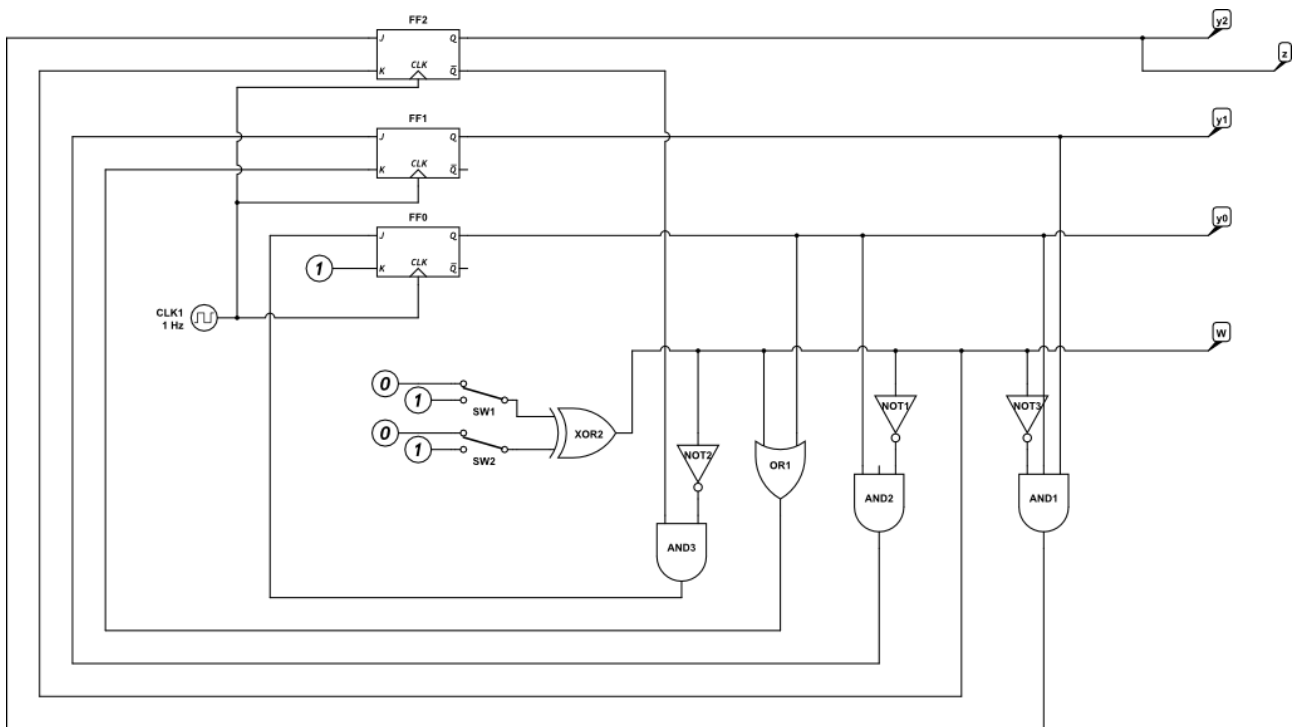


Exercise 8.3

a) We keep partitioning the states until nothing changes:

Initial partition	(ABCDEFGH)
Different outputs	(ACEFG)(BDH)
Second column	(AEG)(C)(F)(B)(D)(H)
Thirrd column	(AG)(E)(C)(F)(B)(D)(H)
No changes.	

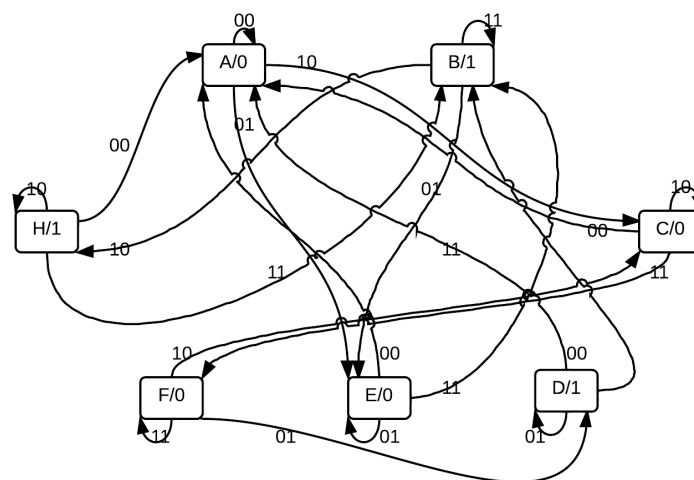That is, only the states *A* and *G* seem to be equivalent. The corresponding state diagram looks as follows:



b) We now number all the states by indices from 000 to 110:

State	In = 00	In = 01	In = 10	In = 11	Output
A = 000	000	100	010	ddd	0
B = 001	ddd	100	110	001	1
C = 010	000	ddd	010	101	0
D = 011	000	011	ddd	001	1
E = 100	000	100	ddd	001	0
F = 101	ddd	011	010	101	0
H = 110	000	ddd	110	001	1

Now one could create three K-Maps for 5 variables (state transitions), one K-Map for 3 variables (mapping from 3 registers to the output), select the prime-implicants, and implement the corresponding circuit with D-Flip-Flops. (Todo, incomplete)