


Technische Informatik: Abgabe 4

Michael Mardaus

Andrey Tyukin

14. November 2013

Exercise 4.1 (Full adder from decoder)

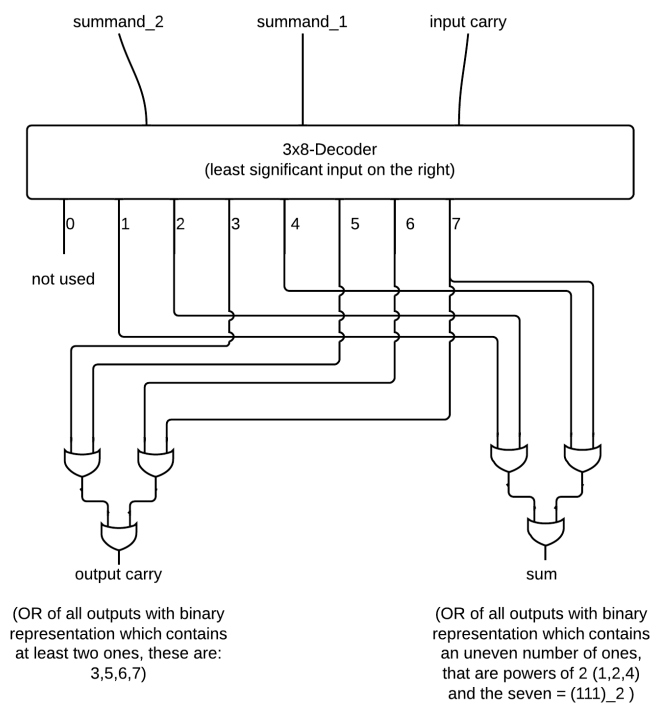

Exercise 4.2 (Subtractors)

a) Here are the tables for the two circuits we wish to implement (namely Half-Subtractor and Full-Subtractor):

minuend	subtrahend	underflow	difference
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0

minuend	subtrahend	underflow	underflow	difference
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

b) More or less compact symbolic representations of these two circuits are as follows (first component is always the resulting underflow, second is the actual difference):

$$HalfSubtractor(m, s) = (\bar{m}s, m \nrightarrow s)$$

$$FullSubtractor(m, s, u) = (\bar{m} \nrightarrow su, m \nrightarrow s \nrightarrow u)$$

c) Now we want to simplify both components (difference and underflow) of the full subtractor using Karnaugh diagrams. We begin with the difference:

		minuend / subtrahend			
		00	01	11	10
underflow	0	?	?	?	?
	1	?	?	?	?

d)

Exercise 4.3 (TODO)

a) b)

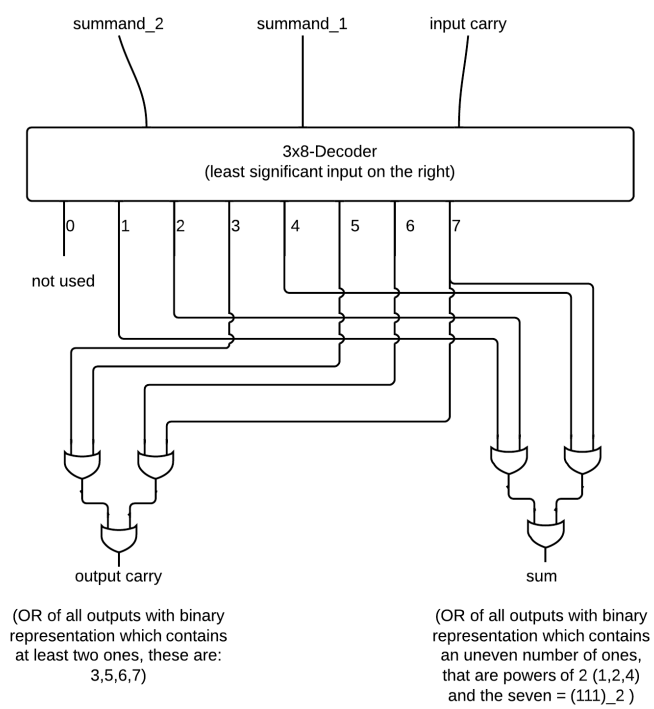


Abbildung 1: Full subtractor. Notice that both outputs share some of the AND gates.