

Technische Informatik: Abgabe 8


Michael Mardaus

Andrey Tyukin

19. Dezember 2013

Exercise 8.1 (JK Flipflop Ringcounter)

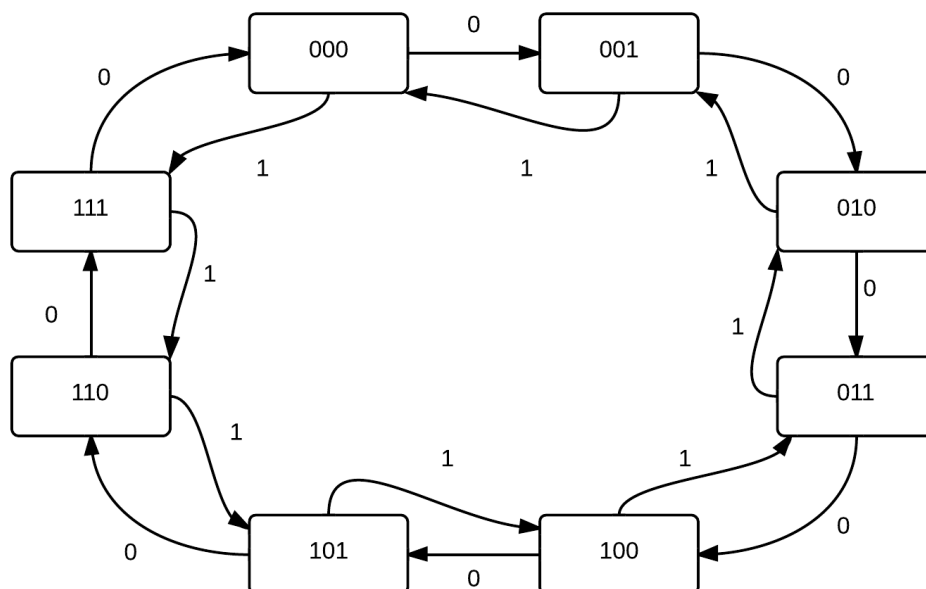a) We want to model a ring-counter that counts forwards if the input w is 0, and backwards if w is 1. It can be modeled by a Moore-automaton (the output depends only on the state). The state diagram looks as follows:




State diagram for the ring-counter. Output is omitted, it's just equal to the node index.

Same in table-form:

State	w = 0	w = 1	Output
000	001	111	000
001	010	000	001
010	011	001	010
011	100	010	011
100	101	011	100
101	110	100	101
110	111	101	110
111	000	110	111


b) The corresponding circuit looks as follows:

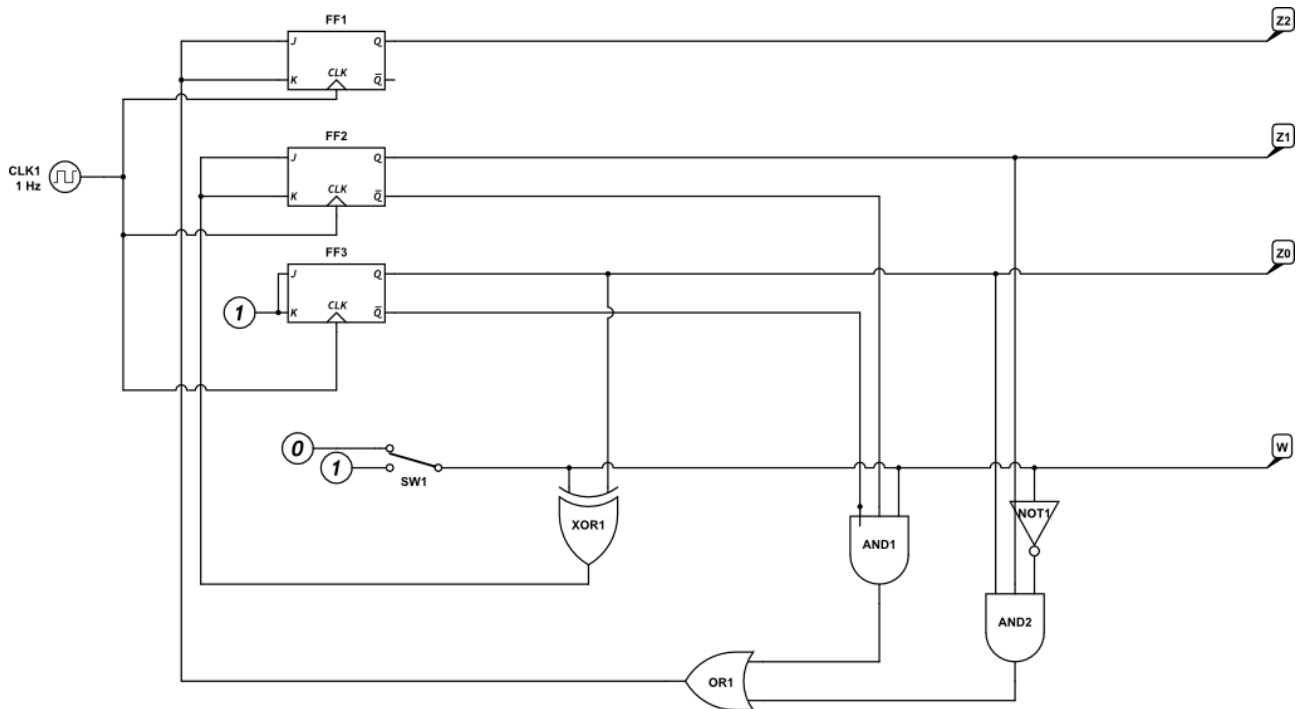

Exercise 8.2 (JK Flipflip for 4 equal inputs)

First we make one input signal w out of the w_1 and w_2 to make the automaton simpler. Therefore we XOR the two signals to one. If both signals are equal XOR makes $w = 0$. If they are different XOR will be $w = 1$. The state diagram for the automaton:

State $y_2y_1y_0$	Next state									Output z
	$w = 0$	$w = 1$	$w = 0$	$w = 1$	$w = 0$	$w = 1$	$w = 0$	$w = 1$	$w = 0$	
000	001	0d	0d	1d	000	0d	0d	0d	0d	0
001	010	0d	1d	d1	000	0d	0d	d1	d1	0
010	011	0d	d0	1d	000	0d	d1	0d	0d	0
011	100	1d	d1	d1	000	0d	d1	d1	d1	0
100	100	d0	0d	0d	000	d1	0d	0d	0d	1
101	ddd	dd	dd	dd	000	dd	dd	dd	dd	d
110	ddd	dd	dd	dd	000	dd	dd	dd	dd	d
111	ddd	dd	dd	dd	000	dd	dd	dd	dd	d

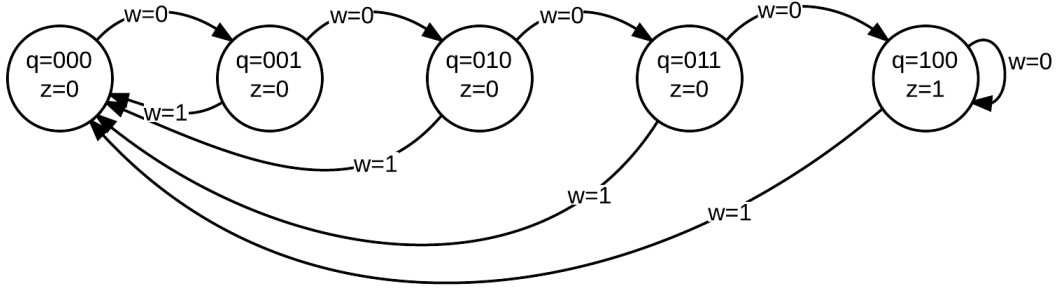

This leads to these K-maps:

J_0 wy_2	y_1y_0			
	00	01	11	01
00	1	d	d	1
01		d	d	d
11		d	d	d
10		d	d	

J_1 wy_2	y_1y_0			
	00	01	11	01
00		1	d	d
01		d	d	d
11		d	d	d
10			d	d

J_2 wy_2	y_1y_0			
	00	01	11	01
00			1	
01	d	d	d	d
11	d	d	d	d
10				

K_0 wy_2	y_1y_0			
	00	01	11	01
00	d	1	1	d
01	d	d	d	d
11	d	d	d	d
10	d	1	1	d


K_1 wy_2	y_1y_0			
	00	01	11	01
00	d	d	1	
01	d	d	d	d
11	d	d	d	d
10	d	d	d	1

K_2 wy_2	y_1y_0			
	00	01	11	01
00	d	d	d	d
01		d	d	d
11	1	d	d	d
10	d	d	d	d

These K-maps lead us to:

$$\begin{aligned}
 J_0 &= \bar{w}\bar{y}_2 \\
 J_1 &= \bar{w}y_0 \\
 J_2 &= \bar{w}y_1y_0 \\
 K_0 &= 1 \\
 K_1 &= w + y_0 \\
 K_2 &= w
 \end{aligned}$$

Which brings us to this circuit:

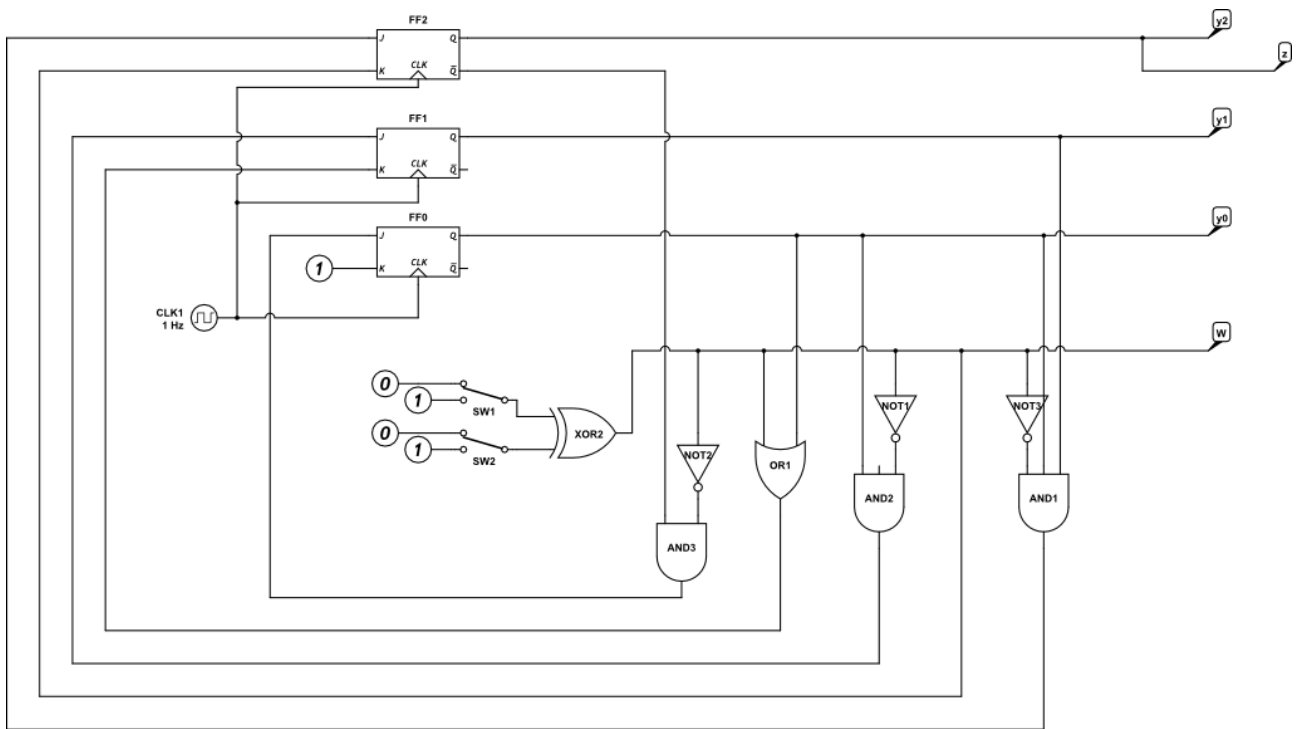

Exercise 8.3 (TODO)

TODO Andrey?