

Technische Informatik: Abgabe 10

Michael Mardaus

Andrey Tyukin

16. Januar 2014

Exercise 10.1 (7-Segment display PLA)

Sorry, but I switched the order to most-significant-bit-first for the inputs.

So in order to be Question-compatible you have to exchange w and z; and x and y here.

Truthtable for LED-display

i	w	x	y	z	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	0	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1
10	1	0	1	0	-	-	-	-	-	-	-
11	1	0	1	1	-	-	-	-	-	-	-
12	1	1	0	0	-	-	-	-	-	-	-
13	1	1	0	1	-	-	-	-	-	-	-
14	1	1	1	0	-	-	-	-	-	-	-
15	1	1	1	1	-	-	-	-	-	-	-

This leads to these K-maps:

a	yz				b	yz				c	yz				d	yz			
wx	00	01	11	10	wx	00	01	11	10	wx	00	01	11	10	wx	00	01	11	10
00	1	0	1	1	00	1	1	1	1	00	1	1	1	0	00	1	0	1	1
01	0	1	1	0	01	1	0	1	0	01	1	1	1	1	01	0	1	0	1
11	d	d	d	d	11	d	d	d	d	11	d	d	d	d	11	d	d	d	d
10	1	1	d	d	10	1	1	d	d	10	1	1	d	d	10	1	0	d	d

e wx	yz				f wx	yz				g wx	yz			
	00	01	11	10		00	01	11	10		00	01	11	10
00	1	0	0	1	00	1	0	0	0	00	0	0	1	1
01	0	0	0	1	01	1	1	0	1	01	1	1	0	1
11	d	d	d	d	11	d	d	d	d	11	d	d	d	d
10	1	0	d	d	10	1	1	d	d	10	1	1	d	d

$$a = w + xz + \bar{x}\bar{z} + yz$$

$$b = \bar{x} + \bar{y}\bar{z} + yz$$

$$c = \bar{y} + z + x$$

$$d = \bar{x}\bar{z} + x\bar{y}z + y\bar{z} + \bar{x}y$$

$$e = \bar{x}\bar{z} + y\bar{z}$$

$$f = w + \bar{y}\bar{z} + x\bar{y} + x\bar{z}$$

$$g = w + \bar{x}y + y\bar{z} + x\bar{y}$$

This gives us this PLA:

input	w	xz	$\bar{x}\bar{z}$	yz	$\bar{y}\bar{z}$	\bar{x}	\bar{y}	z	x	$x\bar{y}z$	$y\bar{z}$	$\bar{x}y$	$x\bar{y}$	$x\bar{z}$	output
w	2	0	0	0	0	0	0	0	0	0	0	0	0	0	
x	0	2	3	0	0	3	0	0	2	2	0	3	2	2	
y	0	0	0	2	3	0	3	0	0	3	2	2	3	0	
z	0	2	3	2	3	0	0	2	0	2	3	0	0	3	
	1	1	1	1	0	0	0	0	0	0	0	0	0	0	a
	0	0	0	1	1	1	0	0	0	0	0	0	0	0	b
	0	0	0	0	0	0	1	1	1	0	0	0	0	0	c
	0	0	1	0	0	0	0	0	0	1	1	1	0	0	d
	0	0	1	0	0	0	0	0	0	0	1	0	0	0	e
	1	0	0	0	1	0	0	0	0	0	0	0	1	1	f
	1	0	0	0	0	0	0	0	0	0	1	1	1	0	g

We can optimize $x = x\bar{z} + xz$ so we could substitute the x column above, so we would only need 13 columns. (I am sure there is more, but for the exercise it is *optimized* now.)


input	w	xz	$\bar{x}\bar{z}$	yz	$\bar{y}\bar{z}$	\bar{x}	\bar{y}	z	$x\bar{y}z$	$y\bar{z}$	$\bar{x}y$	$x\bar{y}$	$x\bar{z}$	output
w	2	0	0	0	0	0	0	0	0	0	0	0	0	
x	0	2	3	0	0	3	0	0	2	0	3	2	2	
y	0	0	0	2	3	0	3	0	3	2	2	3	0	
z	0	2	3	2	3	0	0	2	2	3	0	0	3	
	1	1	1	1	0	0	0	0	0	0	0	0	0	a
	0	0	0	1	1	1	0	0	0	0	0	0	0	b
	0	1	0	0	0	0	1	1	0	0	0	0	1	c
	0	0	1	0	0	0	0	0	1	1	1	0	0	d
	0	0	1	0	0	0	0	0	0	1	0	0	0	e
	1	0	0	0	1	0	0	0	0	0	0	1	1	f
	1	0	0	0	0	0	0	0	0	1	1	1	0	g

10.2 (Von-Neumann adder)

We want to implement the computation unit of a Von-Neumann adder by a PLA. The question is how many columns are required for addition of n -bit numbers.

Claim: The PLA has to have at least $3n$ columns.

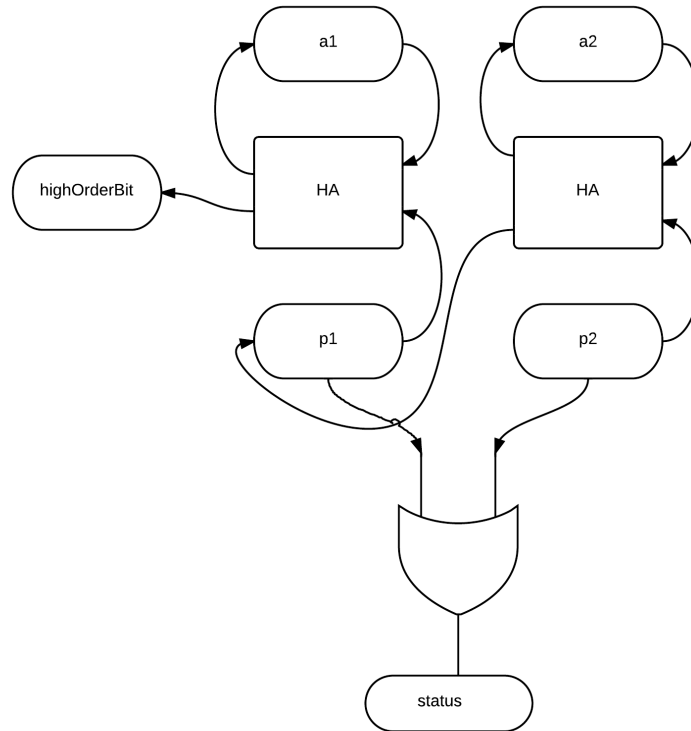Proof: We construct the Von-Neumann adder beginning on the end with the highest order bit carry, and number the delays from left to right, as in the following figure:



Numbering of the registers for the von-Neumann adder is from left to right (CLK omitted)

Recall that the function we wish to implement is defined as follows:

$$\begin{aligned}
 A_i &= a_i \bar{p}_i + \bar{a}_i p_i \\
 P_i &= \begin{cases} a_{i+1} p_{i+1} & \text{for } i < n \\ 0 & \text{for } i = n \end{cases} \\
 \text{highOrderBit} &= a_1 p_1 \\
 \text{status} &= \bigvee_{i=1}^{n-1} a_i p_i
 \end{aligned}$$

Thus, for each new digit we need three new minterms: $\bar{a}_i p_i$, $a_i \bar{p}_i$, $a_i p_i$. Each of these minterms requires one new column in the PLA. The resulting PLA then looks as follows (most zeroes omitted):

a_1	2 3 2	2 3 2			
a_2		2 3 2			
\vdots			\ddots \ddots \ddots		
a_n				2 3 2	
p_1	2 2 3	2 2 3			
p_2		2 2 3			
\vdots			\ddots \ddots \ddots		
p_n				2 2 3	
	0 1 1	0 1 1			A_1
			\ddots \ddots \ddots		A_2
				0 1 1	\vdots
	1 0 0				A_n
		1 0 0			highOrderBit
			\ddots \ddots \ddots		P_1
				1 0 0	\vdots
		1 0 0			P_{n-1}
			\dots \dots \dots	1 0 0	P_n
		1 0 0			status

Thus, the PLA consists of an AND part with $2n \times n$ blocks of size 1×3 and an OR part with $2n \times n$ blocks of size 1×3 . The total number of columns required is therefore $3n$.

Remark: As always, the dot-notation (\ddots) could be rewritten in a more formal inductive argument, but it is questionable whether it would make the explanation shorter or clearer. In this particular case, the dot-notation seemed much more readable.